

DESIGN A PROCESSOR FOR CONTROLLING MIXING PROCESS (CMP)

EEX7436
Processor Design
Assignment 02

by
S.A.P. Kavinda
617143597

Submitted to
Department of Electrical and Computer Engineering
Faculty of Engineering Technology
The Open University of Sri Lanka

at
Colombo Regional Center

on
10/8/2023

Changes done for progress report 01.

Internal Functionality of the Processor

Available Resources in the processor:

#	Type of peripherals	Previous count	Changed Count
1	motor	32	31
2	Vessels	32	31
3	temp. sensors	32	31
4	pressure sensors	32	31
5	concentration sensors	32	31
6	general proposed actuators	64	31
7	general proposed sensors	32	31
8	Profiles	16	16

How the CMP can be used in a mixing machine.


Since Mixing machine has many Actuators to control and many sensors to get inputs, CMP can't control them directly. Also, Actuators and sensors use different protocols and different logic families, needs to convert the CMP's IO pins, as compatible with each actuator and sensors. Drivers are responsible for above both functions. The process of sensor values reading and actuator value providing as follows.

Sensors Value Read: CMP sends the required sensor address to get the sensor output value. Driver will locate the sensor and provide appropriate value to CMP.

Actuator Value Set: Actuator values are needs to be continuously update. When Actuator driver continuously send the required actuator item and the index, CMP provides the respective value.

“Ctr_rst” is uses to reset the CMP and it. When CMP powerd up, It necessarily to be reset. Program memory (RAM) stores the instructions, and operands (Program). CMP fetch the data and execute them by getting program memory data.

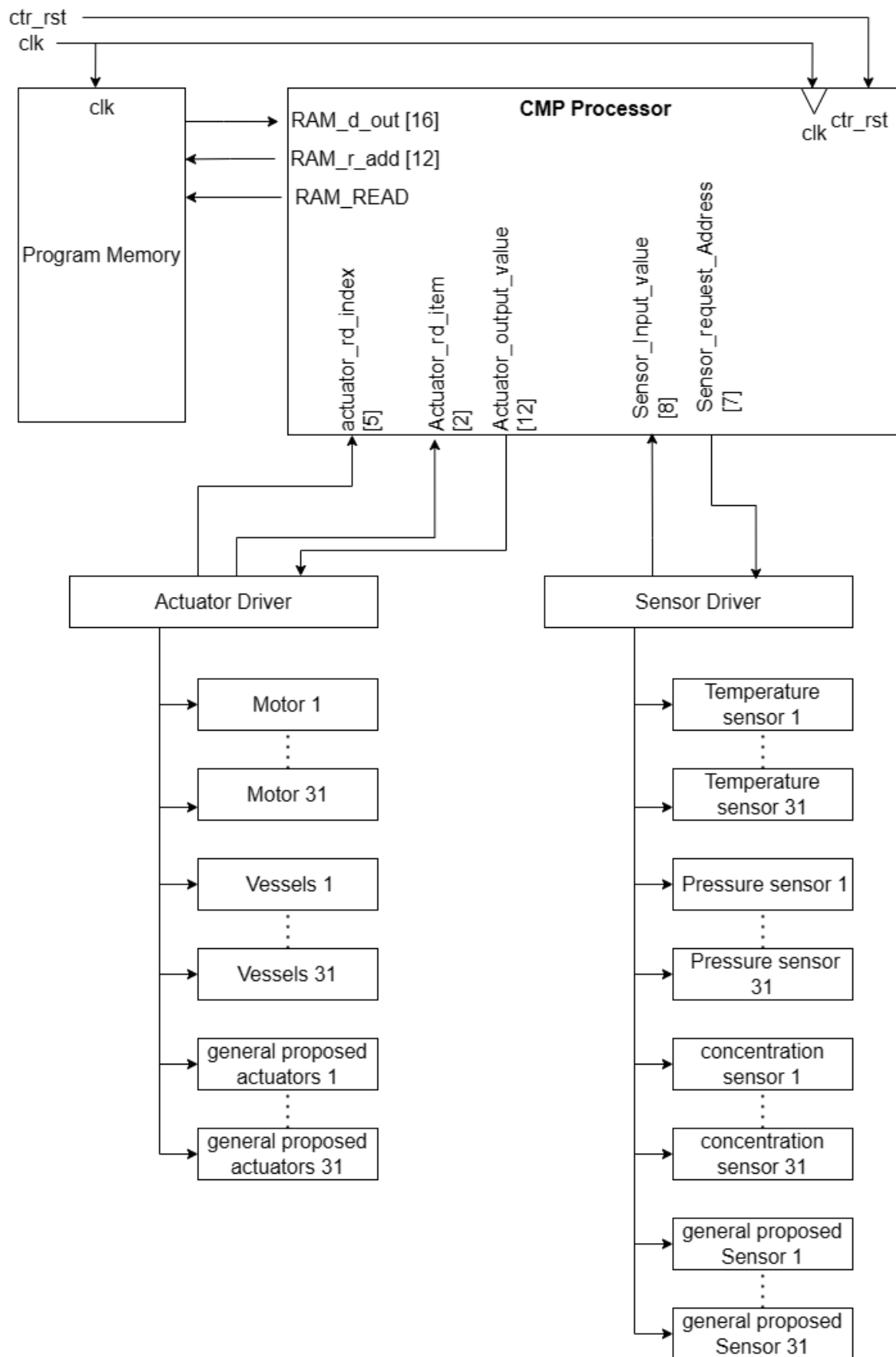This processor used RISC (Reduced Instruction Set Architecture).



Amended ISA

Instruction Word content:

4 bit	12 bit
Opcode	Operands


There are 9 Instructions including reset instruction.

Opcode	Mnemonic	Operands	Bytes	Operation
0XXX	Reset	-	2	Reset the processor to initial state.
Configuration Instructions				
1000	Add2p	P,I,IX	2	Add Items to a Profile ➔ P – Profile Number [4] ➔ I – Item [3] <ul style="list-style-type: none">Outputs:<ul style="list-style-type: none">0 – Motor1 – Vassals2 – General Output3 - NoneInput<ul style="list-style-type: none">4-Temperature sensor5-Pressure sensor6-Concentration sensor7-General Input ➔ IX – Index [5] (0-31) <ul style="list-style-type: none">0 Dedicated to indicates all enable peripheral.
1001	Point	P,I,IX	2	Point to the desired Item before set the values. ➔ P – Profile Number ➔ I – Item ➔ IX – Index *Operands same as Add2P
1010	Setval	V	2	Set the pointed value as given 12-bit value V [12] (0-4095)
Control Instructions				
1011	control	P	2	On Profile Process ➔ P – Profile Number [4]


1100	Findmean	P,I	2	<p>Finding the Mean of given Profile Item List.</p> <p>➔ P – Profile [4]</p> <p>➔ I – Item [2]</p> <ul style="list-style-type: none"> ○ 0-Temperature sensor ○ 1-Pressure sensor ○ 2-concntration sensor ○ 3-General Inputs <p>Store the results in mean register, a 8 Bit register.</p>
1101	compare	V	2	<p>Compare the values with Mean register value, and set the compare flag according to following conditions,</p> $\text{Compare Flag} \begin{cases} 0; V - \text{Mean reg} > 0 \\ 1; V - \text{Mean reg} \leq 0 \end{cases}$ <p>V[8]</p>
1110	JIC	addr	2	<p>Jump if compare flag is 1</p> <p>Addr[12]</p>
1111	waitt	clk	2	<p>Wait given Number of clocks.</p> <p>Clk[12]</p>

Progress Report 02:

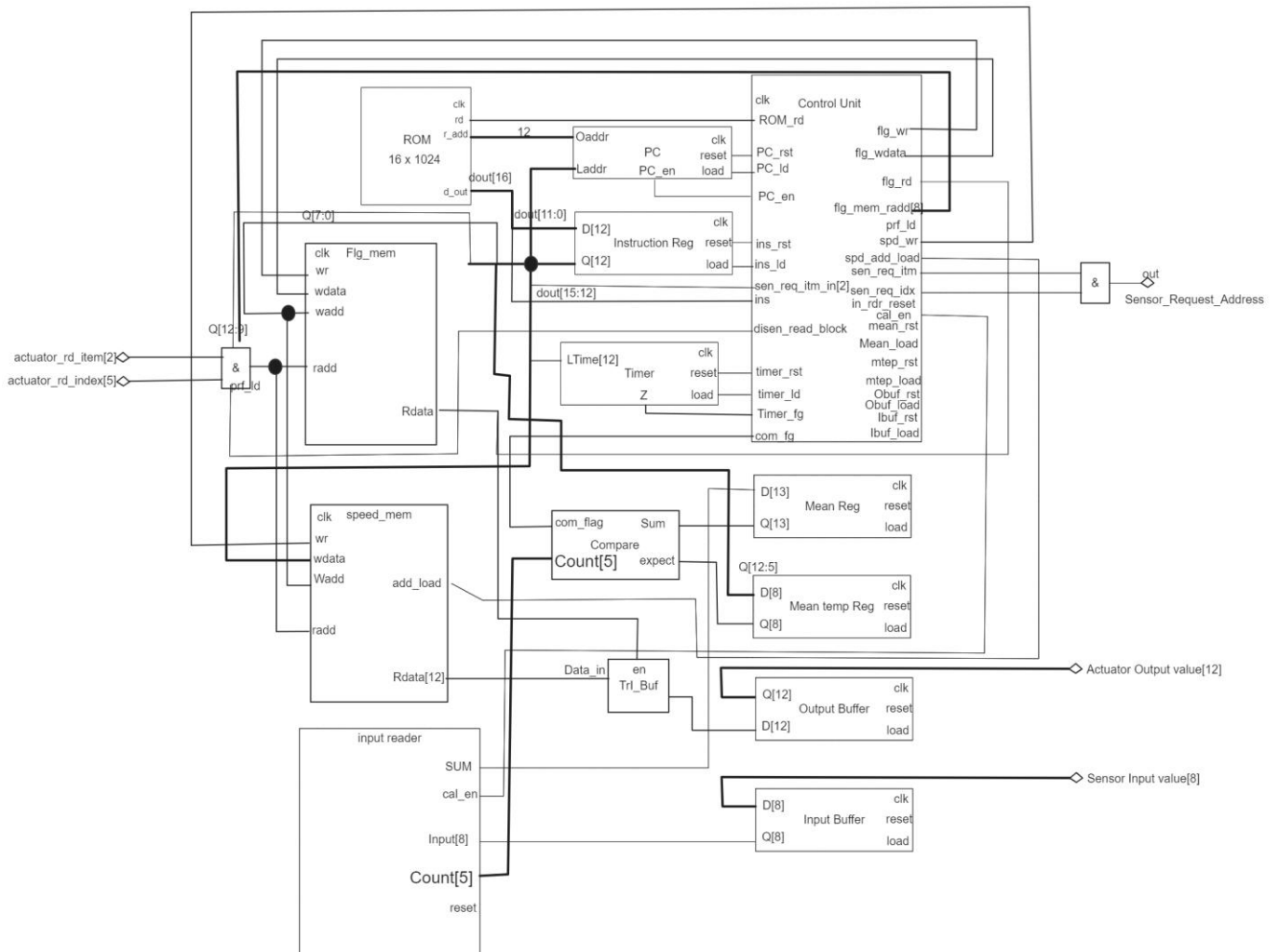1. Draw a block diagram for the processor indicating all input and output signals. Clearly state all functions of each block inside the processor and show the data path.




Program Counter:

 


Used to store and control the address that needs to be fetch next from main memory.

Instruction Register:

 


Used to store the Currently decoding instructions' Operand segments. It store the provide the current operand to the appropriate destination blocks. This data movement control by control unit.

Control unit:

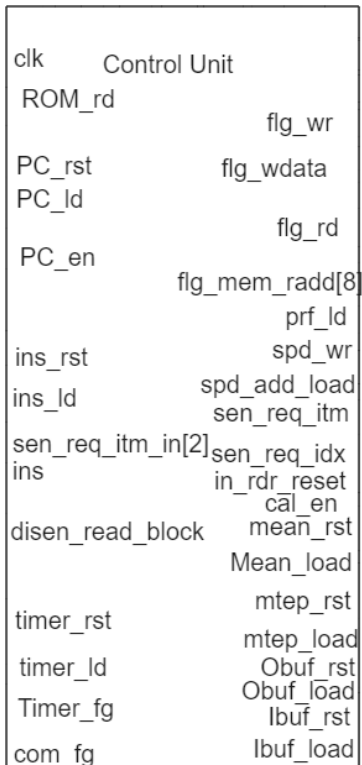


Control Unit Controls the all activities of the processor and it maintain the fetch, decode and execution cycle. It control the all buffers, registers and control the input and output process. Program counter controlling, memory controlling, and control each functions using inbuilt FSM. It maintains the timing and synchronization of each blocks.

Timer

 


Timer used to count the request clock cycles by wait instruction. It is a down counter and control by control unit.

Flag Memory

 


Flag memory used to store the enable actuators and sensors. It is a bit accessible memory unit which has 16 bit width and 12 bit Depth (8 kB). It also can identified the 'all sensors' or 'all actuator' instructions and provides the output accordingly.
(Latency : 1 clock)

Speed Memory

 


Speed Memory used to store the speed values of actuators. It is a 12bit Width and 11 bit depth memory (3 kB). (Latency : 1 clock)

IO Buffers

 

 
IO buffers are used to temporary store the input sensor data and output data until done required operations.




Mean temp and Mean Registers



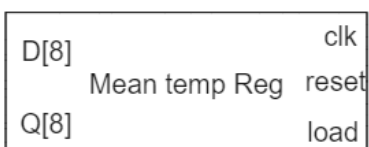Mean temp Register used to store the user provide mean value temporarily until compare. Mean register used to store the calculated mean value. It actually stores the sum of all read values.




Compare Unit

 

Compare unit used to compare the given and calculated mean values. Input reader unit will provide the count of read input values. Therefore, compare unit first multiply the user provided mean value (Mean temp register) by the count. Then it compares with the calculated input values summations (Mean register). Then it provides com_falg as below.

$$\text{Compare Flag} \begin{cases} 0; V - \text{Mean reg} > 0 \\ 1; V - \text{Mean reg} \leq 0 \end{cases}$$

Input Reader

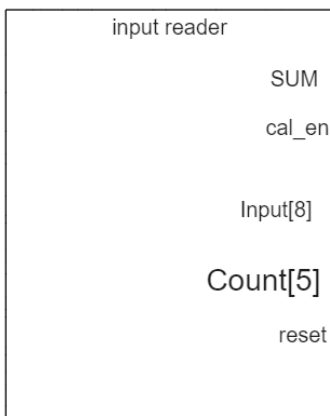

Input reader used to read the sensor values when control unit sends enable signal. It provides the count of read sensor values and the sum of each values.

2. Identify entities for which you need to write VHDL codes to synthesize the processor.

1. Dual Port RAM: Used a Dual port RAM (For both write and read) to store the program. In this assume program is already loaded to memory. Therefore, only add read operation.

Size: 2 kB

Data width: 16 bit

Address Depth: 1024

2. Program Counter: Uses to provide the read address to the memory. Control by control unit and address loaded by instruction register.

Size : 12 bit

3. Instruction Register

Store the Operands temporarily.

Size: 12 bit

4. Compare Block

It compare the two input and provide and bit according to the following logic.

$$\text{Compare Flag} \begin{cases} 0 ; \text{Expect} - \text{Mean} > 0 \\ 1 ; \text{Expect} - \text{Mean} < 0 \end{cases}$$

5. Timer: uses to Count time given clock cycles.

Size: 12 bit

6. Speed memory: A SDRAM register file which use to store the actuator values.

Size: 16x2048 (Need 1536 only)

7. Flg_mem: Uses to store the activation of each profile input/outputs. Defined as a bit accessible memory array.
8. IN/Out buffers: 8 bit and 12 bit Buffers.
9. Mean register, mean temp register
10. Compare unit
11. Input reader unit
12. Tri state buffers
13. Actuator value read address generator
14. Control Unit

3. Write behavioral/ structural VHDL codes for each entity.

- ▼ ● Processor(Pprocessor_arch) (Processor.vhd) (2)
 - ▼ ● No_CTR_sys : proc_no_ctr(proc_no_ctr_arch) (proc_no_ctr.vhd) (13)
 - PC : PC(PC_arch) (PC.vhd)
 - Ins_reg : reg(reg_arch) (reg.vhd)
 - Timer : Timer(Timer_arch) (Timer.vhd)
 - Mean_reg : reg(reg_arch) (reg.vhd)
 - Mean_Temp_Reg : reg(reg_arch) (reg.vhd)
 - Output_Buffer : reg(reg_arch) (reg.vhd)
 - Input_Buffer : reg(reg_arch) (reg.vhd)
 - tri_buf : tri_buf(tri_buf_arch) (tri_buf.vhd)
 - compare : compare(compare_arch) (compare.vhd)
 - Input_Reader : Input_rdr(Input_rdr_arch) (Input_rdr.vhd)
 - Speed_mem : Speed_reg(Speed_reg_arch) (Speed_reg.vhd)
 - Read_addr_gen : Read_addr_gen(Read_addr_gen_arch) (Read_addr_gen.vhd)
 - Flag_mem : flg_mem(flq_mem_arch) (flg_mem.vhd)
 - CONTROL_U : control(control_arch) (Control.vhd)

Program Counter

```
library ieee;
use ieee.std_logic_1164.all;
--use ieee.numeric_std.ALL;
--use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity PC is
generic(
width: integer:=12);
port(
clk,reset,load : in std_logic;
Laddr: in std_logic_vector(width-1 downto 0);
Oaddr: out std_logic_vector(width-1 downto 0);
PC_en: in std_logic);
end entity PC;

architecture PC_arch of PC is

signal Oaddr_TEMP: std_logic_vector(width-1 downto 0);

begin
count_proc: process(clk,reset,load) begin
if(reset = '1') then Oaddr_TEMP<=(others=>'0');
elsif(rising_edge(clk)) then
if(load='1') then Oaddr_TEMP <= Laddr;
elsif(PC_en='1') then Oaddr_TEMP <= Oaddr_TEMP +1;
end if;
end if;
end process;

Oaddr <= Oaddr_TEMP;
end architecture;
```

Register

```
library ieee;
use ieee.std_logic_1164.all;

entity reg is
generic( width: integer:=12);
port(
    clk,reset,load : in std_logic;
    D : in std_logic_vector(width-1 downto 0);
    Q : out std_logic_vector(width-1 downto 0));
end entity reg;

architecture reg_arch of reg is begin
reg_proc: process(clk,load,reset) begin
    if(reset='1') then Q <= (others => '0');
    elsif(rising_edge(clk)) then
        if(load='1') then Q <= D;
        end if; end if;
    end process reg_proc;
end architecture reg_arch;
```

Timer

```
library ieee;
use ieee.std_logic_1164.all;
--use ieee.numeric_std.ALL;
--use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity Timer is
generic(
width: integer:=12);
port(
clk,reset,load : in std_logic;
Ltime: in std_logic_vector(width-1 downto 0);
Z : out std_logic);

end entity Timer;

architecture Timer_arch of Timer is

signal T: std_logic_vector(width-1 downto 0);

begin

Timer_proc: process(clk,reset,load,T) begin
if(reset='1') then T <= (others=>'0');
elsif (rising_edge(clk)) then
    if(load = '1') then T <= Ltime;
    elsif(T /= 0) then T <= T-1;
end if;end if;
end process;

Flag_proc: Process(T) begin
if (T = 0) then Z <= '1';
else Z <= '0';
end if;
end process;

end architecture Timer_arch;
```

Tri-State Buffer

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity tri_buf is
  Port (

    data_in: in std_logic_vector(11 downto 0);
    en: in std_logic;
    tri_out: out std_logic_vector(11 downto 0)
  );
end tri_buf;

architecture tri_buf_arch of tri_buf is

begin
  tri_proc: process(en) is begin
    if(en='1') then tri_out<=data_in;
    else tri_out<=(others=>'Z');
    end if; end process;
end tri_buf_arch;
```

Compare Unit

```
library ieee;
use ieee.std_logic_1164.all;
--use ieee.numeric_std.all;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity compare is
    port (

Expect: in std_logic_vector(7 downto 0);
Sum: in std_logic_vector(12 downto 0);
count: in std_logic_vector(4 downto 0);
com_flag: out std_logic
    );
end entity compare;

architecture compare_arch of compare is
    signal T1,T2,T3,T4,T5,res : std_logic_vector(12 downto 0); -- temp value for
multiplication

begin

mult_proc: process(Expect,count) is begin
    if(count(0)='1') then T1<= ("00000" & Expect ); else T1<=(others=>'0'); end
if;
    if(count(1)='1') then T2<= ("0000" & Expect & "0"); else T2<=(others=>'0');
end if;
    if(count(2)='1') then T3<= ("000" & Expect & "00"); else T3<=(others=>'0');
end if;
    if(count(3)='1') then T4<= ("00" & Expect & "000"); else T4<=(others=>'0');
end if;
    if(count(4)='1') then T5<= ("0" & Expect & "0000"); else T5<=(others=>'0');
end if;
end process;

res <= T1+T2+T3+T4+T5;

Compare_proc: process(res,sum) is begin
    if(res<sum) then com_flag<='0';
    else com_flag<='1';
    end if; end process;

end architecture compare_arch;
```

Input Reader Unit

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity Input_rdr is
port(

    Input: in std_logic_vector(7 downto 0);
    cal_en,reset: in std_logic;
    count: inout std_logic_vector(4 downto 0);
    sum: inout std_logic_vector(12 downto 0)
);
end entity;

architecture Input_rdr_arch of Input_rdr is

begin

read_proc: process(cal_en,reset) begin

if(reset = '1') then
    sum<=(others=>'0');
    count<=(others=>'0');

elsif(cal_en='1') then
    sum <= sum+input;
    count <= count +1;

end if;
end process;

end architecture Input_rdr_arch;
```

Speed Register

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use STD.textio.all;
use IEEE.std_logic_textio.all;
use ieee.numeric_std.ALL;

entity Speed_reg is
generic(
    Dwidth: integer:=12;
    Awidth: integer:=11);
port(
    clk,wr : in std_logic;
    wdata : in std_logic_vector(Dwidth-1 downto 0);
    Wadd_T,RAdd : in std_logic_vector(Awidth-1 downto 0);
    rdata: out std_logic_vector(Dwidth-1 downto 0);
    spd_add_load: in std_logic);

end entity;

architecture Speed_reg_arch of Speed_reg is
type array_type is array(0 to 2**Awidth-1) of std_logic_vector(Dwidth-1 downto 0);

signal array_reg: array_type := (others=>(others=>'0'));
signal Wadd : std_logic_vector(Awidth-1 downto 0);
begin

Addr_buf_proc: process(spd_add_load) begin
    if(spd_add_load = '1') then Wadd <= Wadd_T; end if;
end process;

speed_proc: process(clk,wr,wdata,wadd,radd) begin
if(rising_edge(clk)) then
    if(wr='1') then
        array_reg(to_integer(unsigned(wadd))) <= wdata;
    end if;
    rdata <= array_reg(to_integer(unsigned(radd)));
end if;
end process;
end architecture;
```

Read address Generator

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Read_addr_gen is
  Port (
    Item: in std_logic_vector(1 downto 0);
    Idx: in std_logic_vector(4 downto 0);
    add_out: out std_logic_vector(11 downto 0);
    profile: in std_logic_vector(3 downto 0);
    disable: in std_logic;
    flg_mem_radd: in std_logic_vector(7 downto 0)

  );
end Read_addr_gen;

architecture Read_addr_gen_arch of Read_addr_gen is
  signal profile_T: std_logic_vector(3 downto 0);
  type state_type is (state1,state2);

begin
  --Block_proc: process(disable) is begin

  --if(disable = '0') then add_out <= profile_T & '0' & Item & Idx;
  --elsif(disable = '1') then add_out <= profile & flg_mem_radd; --
  Profile_T<=profile;
  --end if;
  --end process;

  --UPDATE_proc: process(disable) is begin
  --if(disable = '1') then Profile_T<=profile;
  --end if;
  --end process;
  --end Read_addr_gen_arch;
  add_out <= (profile_T & '0' & Item & Idx) when (disable = '0') else
    (profile & flg_mem_radd) when (disable = '1');

  profile_T <= profile when (disable = '1');
end Read_addr_gen_arch;
```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use STD.textio.all;
use IEEE.std_logic_textio.all;
use ieee.numeric_std.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity flg_mem is
generic(
    Dwidth: integer:=16;
    Awidth: integer:=12);
port(
    clk,wr : in std_logic;
    wdata : in std_logic;
    Wadd, radd : in std_logic_vector(Awidth-1 downto 0);
    rdata: out std_logic;
    -- profile: in std_logic_vector(3 downto 0));

end entity;

architecture flg_mem_arch of flg_mem is
type array_type is array(0 to 2**Awidth-1) of std_logic_vector(Dwidth-1 downto 0);

signal array_reg: array_type := (others => (others => '0'));
signal profile_w,profile_r:std_logic_vector(3 downto 0);

begin

write_proc: process(clk,wr,wdata,wadd,radd) begin
if(rising_edge(clk)) then
    if(wr='1') then
        array_reg(to_integer(unsigned(wadd(7 downto 0)))(to_integer(unsigned(profile_w))) <=
wdata; --bit wise acc
    else
        if(radd(7 downto 0)< 32) then
            rdata <= array_reg(to_integer(unsigned(radd(7 downto
0))))(to_integer(unsigned(profile_r))) or array_reg(0)(to_integer(unsigned(profile_r)));

            elsif(radd(7 downto 0) < 64) then
                rdata <= array_reg(to_integer(unsigned(radd(7 downto
0))))(to_integer(unsigned(profile_r))) or array_reg(32)(to_integer(unsigned(profile_r)));

            elsif(radd(7 downto 0) < 96) then
                rdata <= array_reg(to_integer(unsigned(radd(7 downto
0))))(to_integer(unsigned(profile_r))) or array_reg(64)(to_integer(unsigned(profile_r)));

            elsif(radd(7 downto 0) < 128) then
                rdata <= array_reg(to_integer(unsigned(radd(7 downto
0))))(to_integer(unsigned(profile_r))) or array_reg(96)(to_integer(unsigned(profile_r)));

            elsif(radd(7 downto 0) < 160) then
                rdata <= array_reg(to_integer(unsigned(radd(7 downto
0))))(to_integer(unsigned(profile_r))) or array_reg(128)(to_integer(unsigned(profile_r)));

            elsif(radd(7 downto 0) < 192) then
                rdata <= array_reg(to_integer(unsigned(radd(7 downto
0))))(to_integer(unsigned(profile_r))) or array_reg(160)(to_integer(unsigned(profile_r)));

            elsif(radd(7 downto 0) < 224) then
                rdata <= array_reg(to_integer(unsigned(radd(7 downto
0))))(to_integer(unsigned(profile_r))) or array_reg(192)(to_integer(unsigned(profile_r)));

            elsif(radd(7 downto 0) < 256) then
                rdata <= array_reg(to_integer(unsigned(radd(7 downto
0))))(to_integer(unsigned(profile_r))) or array_reg(224)(to_integer(unsigned(profile_r)));

            else rdata <='Z'; end if;
        end if;
    end if;
end process;

profile_w <= Wadd(11 downto 8);
profile_r <= radd(11 downto 8);

end architecture;

```

Control Unit

```
library ieee;
use ieee.std_logic_1164.all;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity control is

port(
clk, ctr_rst : in std_logic;

--Reset Pins
PC_rst,ins_rst,timer_rst, in_rdr_reset,mtep_rst,Obuf_rst: out std_logic;
Ibuf_rst,mean_rst: out std_logic;
spd_add_load: out std_logic;
profile_ld: out std_logic;

--Other control signal pin
ROM_rd,PC_en,PC_ld,disen_read_block,timer_ld,flg_wr : out std_logic;
flg_wdata,spd_wr,cal_en,Mean_load,Obuf_load: out std_logic;
Ibuf_load,mtep_load,ins_ld: out std_logic;

flg_mem_radd : out std_logic_vector(7 downto 0);
sen_req_itm : out std_logic_vector(1 downto 0);
sen_req_idx : out std_logic_vector(4 downto 0);

--External Flags
Timer_fg, com_fg,flg_rd : in std_logic;

--Instrction
ins : in std_logic_vector(3 downto 0);
sen_req_itm_in: in std_logic_vector(5 downto 0)

);
end entity control;

architecture control_arch of control is

type state_type is (Initial,Ideal,Fetch_one,Fetch_two,Decode,Add2p,Point,Setval,
control,Findmean ,compare,JIC,waitt,waitt3,
waitt2,findmean7,Findmean6,findmean5,findmean4,findmean3,findmean22,findmean2,control
_two,setval_two,Setval_three,point_two,add2p_three,Add2p_two);

signal Current_state,Next_state : state_type;
--signal ins_reg : std_logic_vector(3 downto 0);
signal itm: std_logic_vector(1 downto 0);
signal idx: std_logic_vector(4 downto 0);
begin

--ins_reg <= ins;

clk_proc: process(clk,ctr_rst) begin

if(ctr_rst = '1') then
```

```

    Current_state <= Initial;
elsif(rising_edge(clk)) then
    Current_state <= Next_state;
end if;
end process;

Control_proc: process(Current_state,ins,Timer_fg, com_fg )
begin
case (Current_state) is

    When Initial =>
        PC_rst <='1';
        ins_rst <='1';
        timer_rst <='1';
        in_rdr_reset <='1';
        mtep_rst <='1';
        Obuf_rst <='1';
        Ibuf_rst <='1';
        mean_rst <='1';
        spd_add_load <='0';
        Next_state <= Ideal;

    When Ideal =>
        PC_rst <='0';
        ins_rst <='0';
        timer_rst <='0';
        in_rdr_reset <='0';
        mtep_rst <='0';
        Obuf_rst <='0';
        Ibuf_rst <='0';
        mean_rst <='0';

        Next_state <= Fetch_one;

    When Fetch_one =>
        ROM_rd <= '1';
        ins_ld <= '1';
        Mean_load <= '0';
        mtep_load <= '0';
        PC_ld <= '0';
        PC_en <= '0';

        Next_state <= Fetch_two;

    When Fetch_two =>
        Next_state <= Decode;

    When Decode =>
        ROM_rd <='0';
        ins_ld<='0';
--        ins_reg <= ins;

--        if(ins_reg(3)='0') then Next_state<=Initial;

        if(ins = "1000") then Next_state <= Add2p;
        elsif(ins = "1001") then Next_state <= Point;
        elsif(ins= "1010") then Next_state <= Setval;
        elsif(ins="1011") then Next_state<= control;
        elsif(ins = "1100") then Next_state<=Findmean;
        elsif(ins = "1101") then Next_state <= compare;
        elsif(ins = "1110") then Next_state <= JIC;
        elsif(ins = "1111") then Next_state <= waitt;
        else Next_state <= Initial;
        end if;

```



```

idx <= "00000";

PC_en <= '1';
Next_state <= Findmean2;

when Findmean2 =>
    cal_en<='0';
    PC_en <= '0';

    if(idx = "11111") then
        disen_read_block <= '0';
        Next_state <= Fetch_one;
        Mean_load <= '1';
    else
        flg_mem_radd <= '1' & itm & idx;
        Next_state <= findmean22;
    end if;

When Findmean22 =>
    Next_state <= Findmean3;

When Findmean3 =>

    if(flg_rd = '1') then
        sen_req_itm <= itm;
        sen_req_idx <= idx;
        Next_state <= Findmean4;
    else
        idx <= idx +1;
        Next_state <= Findmean2;
    end if;

When Findmean4 =>
    Next_state <= findmean5;

When Findmean5 =>
    Ibuf_load <= '1';
    Next_state <= Findmean6;

When findmean6 =>
    Next_state <= Findmean7;

when findmean7 =>
    Next_state <= Findmean2;
    cal_en <= '1';
    idx <= idx+1;

-----Compare-----

When compare =>
    mtep_load <= '1';
    Next_state <= Fetch_one;
    PC_en <= '1';

when JIC =>

    if(com_fg = '1') then
        PC_ld <= '1';
        Next_state <= Fetch_one;
    else
        PC_en <= '1';
        Next_state <= Fetch_one;
    end if;

when Waitt =>
    timer_ld <= '1';

```

```

        Next_state <= waitt2;

    when Waitt2 =>
        Next_state <= waitt3;

    when waitt3 =>
        timer_ld <= '0';
        if(Timer_fg = '1') then
            Next_state <= Fetch_one;
            PC_en <= '1';
        end if;

    When others=>
        Next_state <= Initial;

    end case;

end process control_proc;

end architecture Control_arch;

```

4. Give a complete VHDL code for the processor.

By including all components without control unit, created no_ctr.vhd model. Processor consists of both no_ctr and control unit.

----- NO CONTROL UNIT-----

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity proc_no_ctr is

generic(
w_12 :integer:=12;
w_13 : integer:=13;
w_8  : integer:=8;
w_11 : integer:=11;
w_16 : integer:=16
);

Port (
clk: in std_logic;

--Contrl unit signals-----//*****
PC_rst,PC_ld, ins_rst,ins_ld,timer_rst,timer_ld,flg_wr,flg_wdata,PC_en : in
std_logic;
spd_wr,in_rdr_reset,cal_en,mean_rst,mean_load,mtep_rst,disen_read_block : in
std_logic;
mtep_load,obuf_rst,obuf_load,ibuf_rst,ibuf_load,rom_rd : in std_logic;
spd_add_load: in std_logic;
sen_req_itm_in:out std_logic_vector(5 downto 0);

ins : out std_logic_vector(3 downto 0);
timer_fg,com_fg,flg_rd : out std_logic;

```



```

sen_req_itm: in std_logic_vector(1 downto 0);
sen_req_idx: in std_logic_vector(4 downto 0);
flg_mem_radd: in std_logic_vector(7 downto 0);

--Main memory in out -----///*
Rom_read: out std_logic;
Rom_r_add: out std_logic_vector(11 downto 0);
ROM_d_out: in std_logic_vector(15 downto 0);

--Inout pins -----///*
actuator_rd_item: in std_logic_vector(1 downto 0);
actuator_rd_index: in std_logic_vector(4 downto 0);
Sensor_rqst_address: out std_logic_vector(6 downto 0);
Actuator_output_value: out std_logic_vector(11 downto 0);
Sensor_Input_value: in std_logic_vector(7 downto 0)
);
end proc_no_ctr;

architecture proc_no_ctr_arch of proc_no_ctr is

signal ins_reg_Q,radd_s,output_D,spd_read_data: std_logic_vector(11 downto 0);
signal sum_D,Sum_Q: std_logic_vector(12 downto 0);
signal expect_s,count_input:std_logic_vector(7 downto 0);
signal Flg_RData: std_logic;
signal count: std_logic_vector(4 downto 0);
signal Wadd_signal,Radd_signal : std_logic_vector(10 downto 0);

begin

PC: entity work.PC(PC_arch) --checked
generic map(width => w_12)
port map(clk=>clk,PC_en=>PC_en,reset =>
PC_rst,load=>PC_ld,Oaddr=>ROM_r_add,Laddr=>INS_REG_Q);

Ins_reg: entity work.Reg(Reg_arch) --checked
generic map(width => w_12)
port map(clk=>clk,reset=>ins_rst,load=>ins_ld,D=>ROM_d_out(11 downto
0),Q=>ins_reg_Q);

Timer: entity work.Timer(Timer_arch) --checked
generic map(width=>w_12)
port map(clk=>clk,reset=>timer_rst,load=>Timer_ld,Ltime=>ins_reg_Q,Z=>timer_fg);

Mean_reg: entity work.Reg(Reg_arch) --checked
generic map(width => w_13)
port map(clk=>clk,reset=>mean_rst,load=>mean_load,D=>sum_D,Q=>Sum_Q);

Mean_Temp_Reg: entity work.Reg(Reg_arch) --checked
generic map(width => w_8)
port map(clk=>clk,reset=>mtep_rst,load=>mtep_load,Q=>expect_s,D=>ins_reg_Q(11 downto
4));

Output_Buffer: entity work.Reg(Reg_arch) --checked
generic map(width => w_12)
port
map(clk=>clk,reset=>obuf_rst,load=>obuf_load,D=>output_D,Q=>Actuator_output_value);

Input_Buffer: entity work.Reg(Reg_arch) --checked
generic map(width => w_8)
port
map(clk=>clk,reset=>ibuf_rst,load=>ibuf_load,D=>Sensor_Input_value,Q=>count_input);

tri_buf: entity work.tri_buf(tri_buf_arch) --checked
port map(data_in=>spd_read_data, en=>Flg_RData, tri_out=>output_D);

```

```

compare: entity work.compare(compare_arch) --checked
port map(Expect=>expect_s, Sum=>Sum_Q, count=>count ,com_flag=>com_fg);

Input_Reader: entity work.Input_rdr(Input_rdr_arch) --checked
port map(Input=>count_input,
Cal_en=>cal_en,reset=>in_rdr_reset,count=>Count,sum=>Sum_D);

Speed_mem: entity work.Speed_reg(speed_reg_arch) --checked
Generic map (Dwidth=>W_12, Awidth=>w_11)

port map(clk=>clk,wr=>spd_wr,Wdata=>ins_reg_Q
,Wadd_T=>Wadd_signal,Radd=>Radd_signal,rdata=>spd_read_data,spd_add_load=>spd_add_load);

Read_addr_gen: entity work.Read_addr_gen --checked
port
map(Item=>actuator_rd_item,flg_mem_radd=>flg_mem_radd,Idx=>actuator_rd_index,add_out=>radd_s,profile=>ins_reg_Q(11 downto 8),disable=>disen_read_block);

Flag_mem: entity work.flg_mem
generic map(Dwidth=>w_16,Awidth=>w_12)
port
map(clk=>clk,wr=>flg_wr,wdata=>flg_wdata,wadd=>ins_reg_Q,radd=>radd_s,rdata=>Flg_RData);

Wadd_signal <= (ins_reg_Q(11 downto 8) & ins_reg_Q(6 downto 0));
Radd_signal <= (radd_s(11 downto 8) & radd_s(6 downto 0));
Rom_read <= rom_rd;
flg_rd <= Flg_RData;
Sensor_rqst_address <= sen_req_itm & sen_req_idx;
ins <= ROM_d_out(15 downto 12);
--radd_s <= ins_reg_Q(11 downto 8) & flg_mem_radd;
sen_req_itm_in <= ins_reg_Q(5 downto 0);

end proc_no_ctr_arch;

```

-----TOP MODULE – PROCESSOR-----

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Processor is
    generic(
        w_12 : integer:=12;
        w_13 : integer:=13;
        w_8  : integer:=8;
        w_11 : integer:=11;
        w_16 : integer:=16
    );

    Port (

        clk : in std_logic;

        --Memory Control pin
        ROM_read : out std_logic; --ok
        ROM_r_add : out std_logic_vector(11 downto 0); --ok
        ROM_d_out : in std_logic_vector(15 downto 0); --ok

        --IO pin
        actuator_rd_item : in std_logic_vector(1 downto 0); --ok
        actuator_rd_index : in std_logic_vector(4 downto 0); --ok
        Sensor_input_value : in std_logic_vector(7 downto 0); --ok

        Actuator_output_value : out std_logic_vector(11 downto 0); --ok
        Sensor_Request_Address : out std_logic_vector(6 downto 0); --ok

        --Reset control unit
        ctr_rst : in std_logic

    );
end Processor;

architecture Processor_Arch of Processor is
    --Internal control paths

    signal PC_rst,PC_ld, ins_rst,ins_ld,timer_rst,timer_ld,flg_wr,flg_wdata,PC_en :
    std_logic;
    signal spd_wr,in_rdr_reset,cal_en,mean_rst,mean_load,mtep_rst,disen_read_block :
    std_logic;
    signal mtep_load,obuf_rst,obuf_load,ibuf_rst,ibuf_load,rom_rd,spd_add_load :
    std_logic;

    signal ins : std_logic_vector(3 downto 0);
    signal timer_fg,com_fg,flg_rd : std_logic;
    signal sen_req_itm: std_logic_vector(1 downto 0);
    signal sen_req_idx: std_logic_vector(4 downto 0);
    signal flg_mem_radd: std_logic_vector(7 downto 0);
    signal sen_req_itm_in: std_logic_vector(5 downto 0);

begin

    No_CTR_sys: entity work.proc_no_ctr(proc_no_ctr_arch)
    generic map(w_12=>w_12,w_13=>w_13,w_8=>w_8,w_11=>w_11,w_16=>w_16)
    port map(
        --Control unit signals
        clk=>clk,PC_rst => PC_rst,PC_ld => PC_ld, ins_rst => ins_rst,ins_ld => ins_ld,
```

```

timer_rst => timer_rst, timer_ld =>
timer_ld, flg_wr => flg_wr, flg_wdata => flg_wdata, PC_en => PC_en,
spd_wr => spd_wr, in_rdr_reset => in_rdr_reset, cal_en => cal_en, mean_rst => mean_rst,
mean_load => mean_load, mtep_rst => mtep_rst, disen_read_block => disen_read_block,
mtep_load => mtep_load, obuf_rst => obuf_rst, obuf_load => obuf_load, ibuf_rst => ibuf_rst,
ibuf_load => ibuf_load, rom_rd => rom_rd, spd_add_load => spd_add_load, sen_req_itm_in => sen_req_itm_in,

ins => ins,
timer_fg => timer_fg, com_fg => com_fg, flg_rd => flg_rd,
sen_req_itm => sen_req_itm,
sen_req_idx => sen_req_idx,
flg_mem_radd => flg_mem_radd,

--Main Memory in out
Rom_read => ROM_read,
Rom_r_add => ROM_r_add,
ROM_d_out => ROM_d_out,

--Input Pins
actuator_rd_item => actuator_rd_item,
actuator_rd_index => actuator_rd_index,
Sensor_rqst_address => Sensor_Request_Address,
Actuator_output_value => Actuator_output_value,
Sensor_Input_value => Sensor_input_value

);

CONTROL_U: entity work.control(control_arch)
port map(

--Reset Pins and clocks
clk => clk, ctr_rst => ctr_rst, PC_rst => PC_rst, ins_rst => ins_rst, timer_rst => timer_rst,
in_rdr_reset => in_rdr_reset, mtep_rst => mtep_rst, Obuf_rst => Obuf_rst,
Ibuf_rst => Ibuf_rst, mean_rst => mean_rst, spd_add_load => spd_add_load, sen_req_itm_in => sen_req_itm_in,

--Other control signal pin
ROM_rd => ROM_rd, PC_en => PC_en, PC_ld => PC_ld, disen_read_block => disen_read_block,
timer_ld => timer_ld, flg_wr => flg_wr,
flg_wdata => flg_wdata, flg_rd => flg_rd, spd_wr => spd_wr, cal_en => cal_en,
Mean_load => Mean_load, Obuf_load => Obuf_load,
Ibuf_load => Ibuf_load, mtep_load => mtep_load, ins_ld => ins_ld,

flg_mem_radd => flg_mem_radd,
sen_req_itm => sen_req_itm,
sen_req_idx => sen_req_idx,

--External Flags
Timer_fg => Timer_fg, com_fg => com_fg,

ins => ins


);

end Processor_Arch;

```

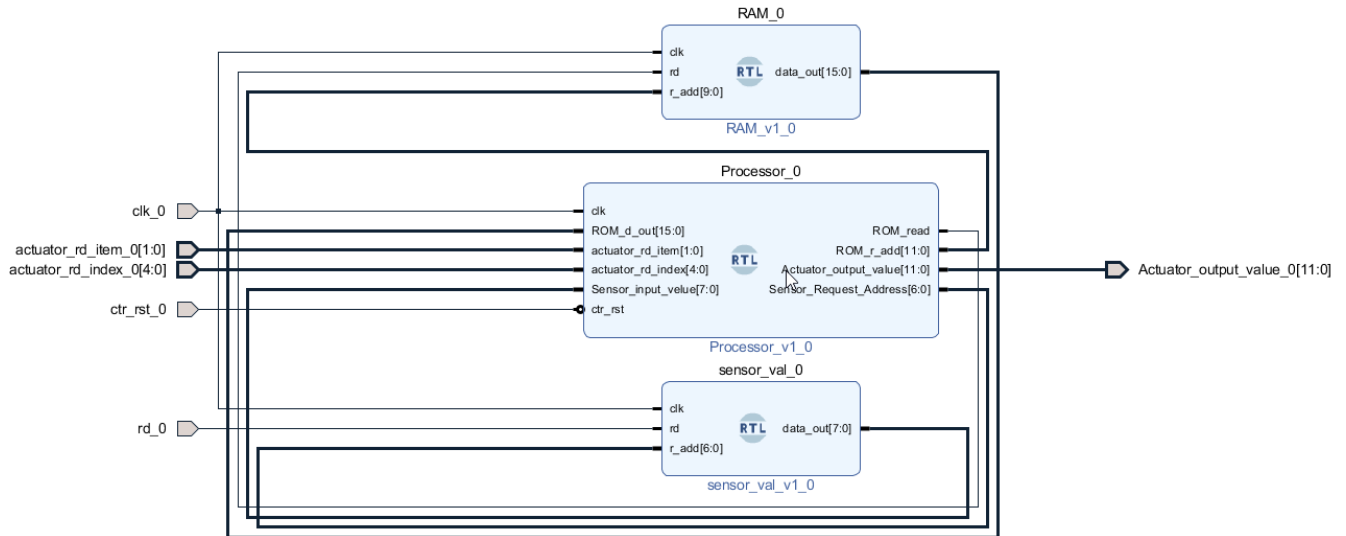5. Draw timing diagrams to realize the instructions of the processor you have designed.

To simulate the processor functionality and make Timing diagrams, create a Test setup as follows.



Here, RAM initialized with this program:

```
1000 0001 000 00010 -- ADD2P 1 0 3 ;Add motor 2 to profile 1
1000 0001 000 00011 -- ADD2P 1 0 4 ;Add motor 3 to profile 1
1000 0001 100 00000 -- ADD2P 1 0 0 ;Add all temp sensor to profile 1
1001 0001 000 00010 -- Point 1 0 2 ;Point to motor2 profile1
1010 0011111111111 -- Setval 511 ; Set value 511 to located point
1001 0001 000 00011 -- Point 1 0 3 ;Point to motor3 profile 1
1010 0010011100001 -- Setval 625 ; Set value 625 to located point
1011 0000000000001 -- Control 1 ; Start profile 1
1111 0000000000111 -- Waitt 7 ; wait 7 clocks
1100 0001000000000 -- Findmean 1,0 ;Find mean val of all temp sensor
1101 0000110010000 -- compare 200 ; find the mean >200
1110 0000000001001 -- JIC 9 ; if mean > given vale, jump to 8
0000 0000000000000 -- Reset ; reset
```


To demonstrate the Sensor values, use another memory element. It act as a sensor driver and provide sensor read value. To verification purpose, initialized this RAM randomly using below python snippet.

```
import numpy as np
file = open("sensor_val.txt", "w")


for j in range(0, 2**7):
    bval = np.random.randint(2, size=8)
    print(bval)
    for i in range(0, 8):
        file.write(str(bval[i]))
    file.write("\n")

file.close()
```

 
1. Initially control unit set all registers to reset state(0 state).




2. Fetch & Decode

 



3. Add2P

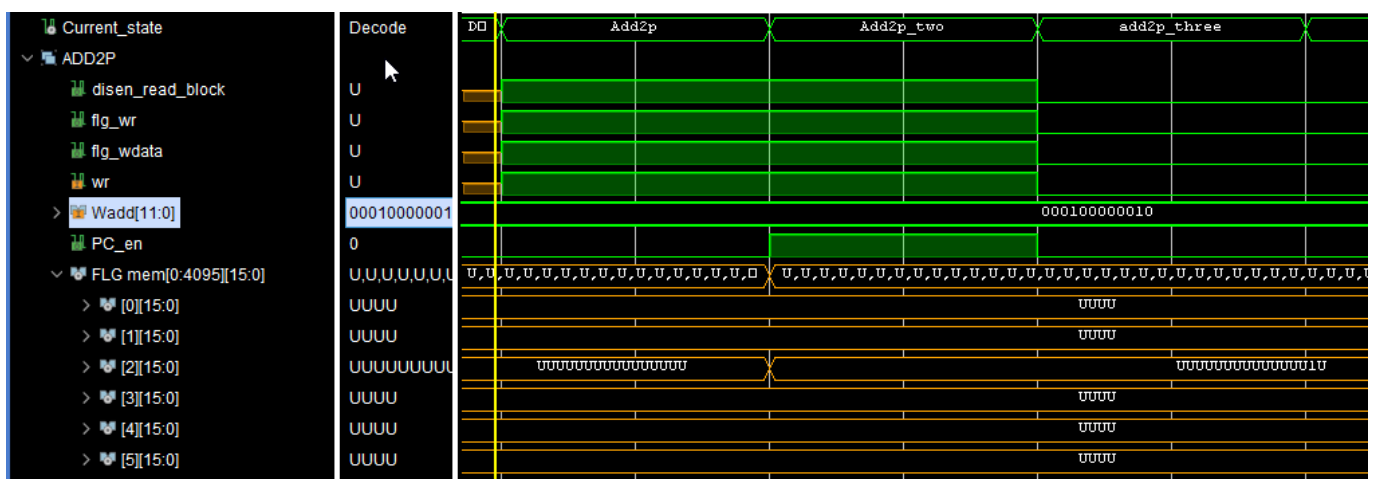

 
After add motor 2,3 and all temp sensors, the flag memory consists as this,




4. Point and Setval

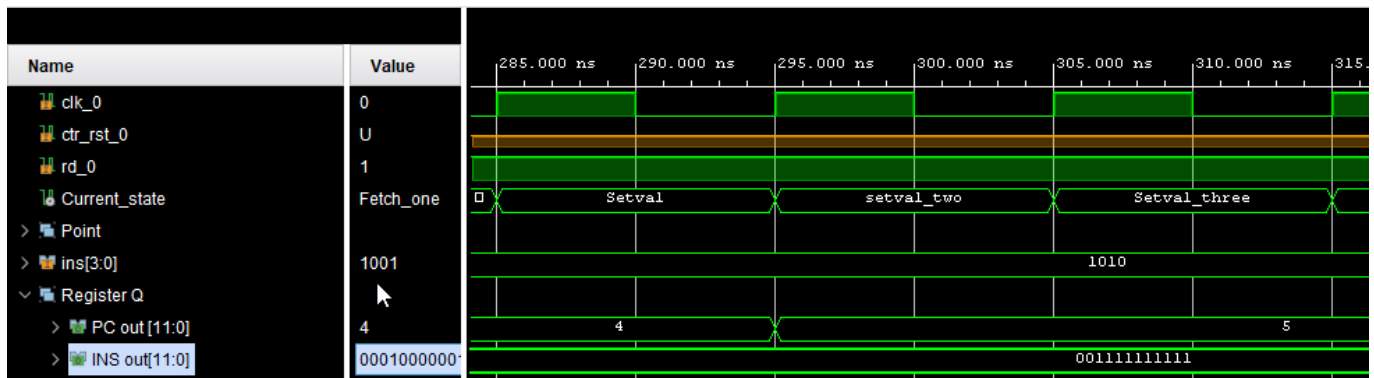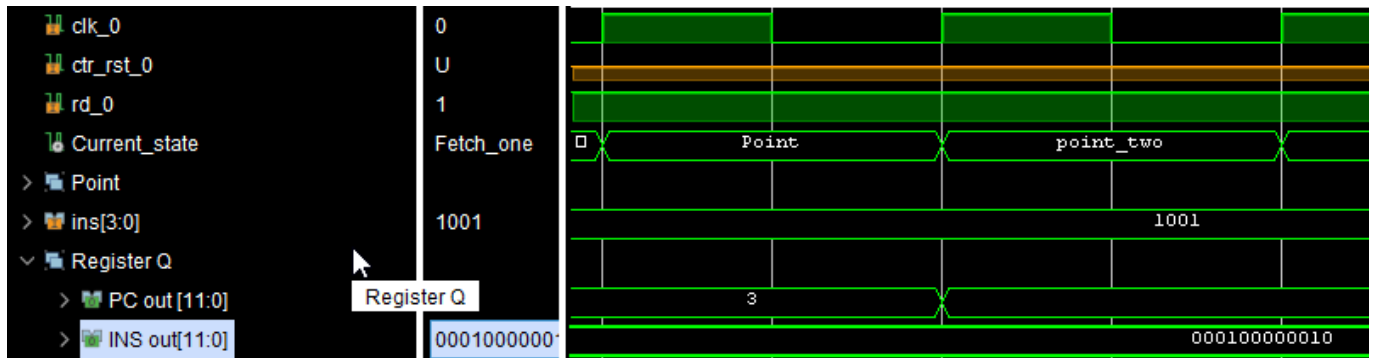

 After the point and setval instructions, these are the speed memory content,




5. Waitt

 

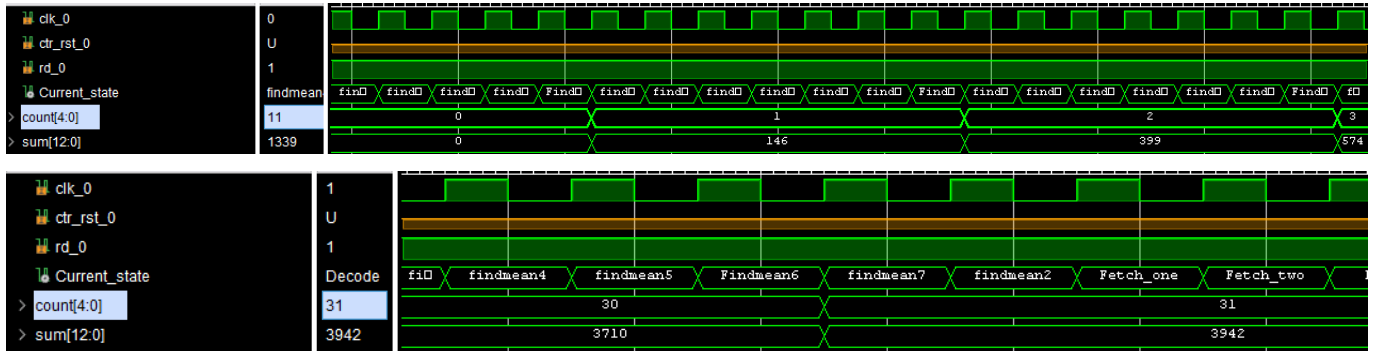
6. Findmean

Findmean is the most computationally expensive operation in this processor. It summing up all the enabled sensor values and locate them in mean register.



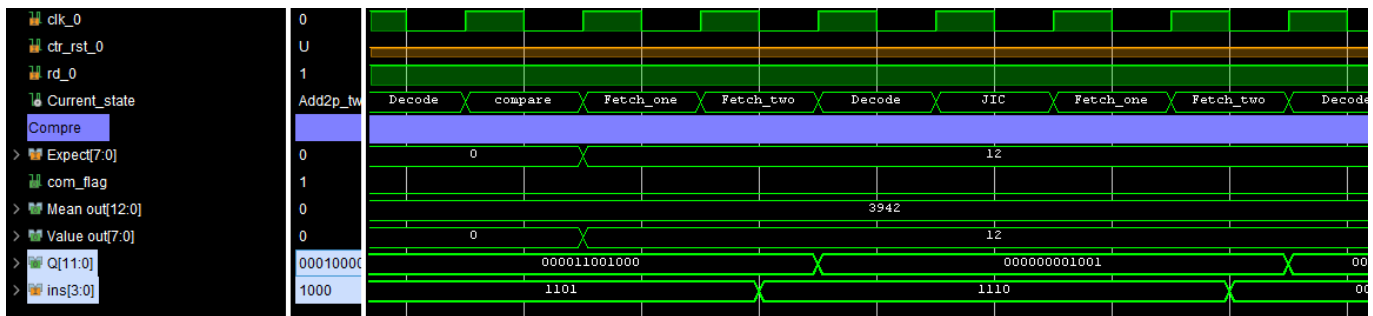7. Comapre & JIC

Check the mean value < Expected value. If true, go to given address. Else continue. In this example condition was true.



8. Reset

Reset to the Initial stage.

Reset processor to initial stage.

